
DSM
IIT Hyderabad

October 2024

Time: 45 min

Quiz-2 Exam

Maximum Marks: 20

Set A

Answer all the questions.

Answer in the space provided only.

All the best

Roll Number:

Seat Number:

Room Number:

Invigilator signature:

Question number	Marks (a)	Marks (b)	Marks (c)	Marks (d)	Name of TA corrected
1					
2					
3					
4					
5					
6					
Total					

No reading material is allowed to use in the exam hall.

No exchange of material during exam.

Use back sheets for rough work. No additional papers for rough work / answers.

Answer in the space provided only.

1. A stream of bits is given as input, and we need to detect a double zero (two consecutive zeros). You have JK FF and some basic logic gates available.
 - (a) Draw a state (transition) diagram [2M]
 - (b) Complete state table [2M]
 - (c) Implement simplest circuit which will achieve double zero detection [5M]

contd..

contd..

2. Describe using a few words or diagram
- (a) Compare SR latch vs JK flipflop [2 M]
 - (b) Shift register vs Parallel register with Pros & Cons. [2M]
 - (c) Equivalent states [1M]
 - (c) Synchronous reset [1M]

contd..

contd..

3. Design a 4-bit universal shift register using T flip-flops and explain its operation. [5 M]

contd..

Rough work